

Chapter 2

Logic Functions and Gates

ECET 331 – Digital Integrated Circuits

Basic Logic Functions

- Three Basic Logic Functions
 - AND
 - OR
 - NOT
- Other functions can be created from these

ECET 331 - Digital Integrated Circuits

Logic Function Representation

- Logic functions can be represented:
 - Algebraically
 - Using truth tables
 - Using electronic circuits

ECET 331 - Digital Integrated Circuits

Algebraic Representation

- Uses Boolean algebra
- Boolean variables have two states (binary)
- Boolean operators include:
 - AND
 - OR
 - NOT

ECET 331 - Digital Integrated Circuits

Truth Table Representation

- Defines the output of a function for every possible combination of inputs
- A system with n inputs has 2^n possible combinations

ECET 331 - Digital Integrated Circuits

Electronic Circuit Representation

- Uses logic *gates* to perform Boolean algebraic functions
- Gates can be represented by schematic symbols
- Symbols can be either distinctive-shape or rectangular-outline

ECET 331 - Digital Integrated Circuits

Distinctive Shape Schematic Symbols

- Uses different graphic representations for different logic functions
- Uses a bubble (a small circle) to indicate a logical inversion

ECET 331 - Digital Integrated Circuits

Rectangular-Outline Schematic Symbols

- All functions are shown in rectangular form with the logic function indicated by standard notation inside the rectangle
- The notation specifying the logic function is called the qualifying symbol
- Inversion is indicated by a 1/2 arrowhead

ECET 331 - Digital Integrated Circuits

NOT Function

- One input and one output
- The output is the opposite logic level of the input
- The output is the complement of the input

ECET 331 - Digital Integrated Circuits

NOT Function Boolean Representation

- Inversion is indicated by a bar over the signal to be inverted

$$Y = \bar{A}$$

Truth Table

A	Y
0	1
1	0

ECET 331 - Digital Integrated Circuits

NOT Function Electronic Circuit

- Called a **NOT gate** or, more usually, an **Inverter**
- Distinctive-shape symbol uses a triangle with inversion bubble



ECET 331 - Digital Integrated Circuits

NOT Function Electronic Circuit

- Rectangular symbol uses "1" and the inversion half arrowhead (IEEE std. 91-1984)



ECET 331 - Digital Integrated Circuits

AND Function

- Two or more inputs, one output
- Output is HIGH only when all of the inputs are HIGH
- Output is LOW whenever any input is LOW
- *Logical Product*

ECET 331 - Digital Integrated Circuits

AND Boolean Representation

- AND symbol is “•” or nothing at all

$$Y = A \cdot B$$

$$Y = AB$$

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

ECET 331 - Digital Integrated Circuits

AND Function Electronic Circuit

- Called an *AND gate*
- Distinctive-shape symbol uses AND designation
- Rectangular-shape symbol use “&” as designator



a. Distinctive-shape



b. Rectangular-outline

ECET 331 - Digital Integrated Circuits

OR Function

- Two or more inputs, one output
- Output is HIGH whenever one or more input is HIGH
- Output is LOW only when all of the inputs are LOW
- *Logical Sum*

ECET 331 - Digital Integrated Circuits

OR Boolean Representation

- OR symbol is “+”
- $Y = A + B$


Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


ECET 331 - Digital Integrated Circuits

OR Function Electronic Circuit

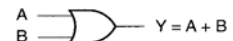- Called an *OR gate*
- Distinctive-shape symbol uses OR designation
- Rectangular-shape symbol uses “≥” as designator



a. Distinctive-shape

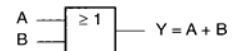

b. Rectangular-outline

ECET 331 - Digital Integrated Circuits

Active Level

- The logic level defined as “ON” for a circuit
- When a logic HIGH is “ON”, the signal is **active-HIGH**
- When a logic LOW is “ON”, the signal is **active-LOW**
 - Indicated by a bubble at the output terminal of the logic function

ECET 331 - Digital Integrated Circuits

NAND Function

- Generated by inverting the output of the AND function
- Output is HIGH whenever any input is LOW
- Output is LOW only when all inputs are HIGH

ECET 331 - Digital Integrated Circuits

NAND Boolean Representation

- Uses AND with an inversion overbar

$$Y = \overline{A \cdot B}$$

$$Y = \overline{AB}$$

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

ECET 331 - Digital Integrated Circuits

NAND Function Electronic Circuit

- Called a **NAND gate**
- Uses the AND symbol with inversion on the output



ECET 331 - Digital Integrated Circuits

NOR Function

- Generated by inverting the output of the OR function
- Output is HIGH only when all inputs are LOW
- Outputs is LOW whenever any input is HIGH

ECET 331 - Digital Integrated Circuits

NOR Boolean Representation

- Uses OR with an inversion overbar

$$Y = \overline{A + B}$$

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

ECET 331 - Digital Integrated Circuits

NOR Function Electronic Circuit

- Called a **NOR gate**
- Uses OR symbol with inversion on the output



ECET 331 - Digital Integrated Circuits

Exclusive OR Gate


- Two inputs, one output
- Output is HIGH when one, and only one, input is HIGH
- Output is LOW when both inputs are equal – both HIGH or both LOW

$$Y = A \oplus B = A\bar{B} + \bar{A}B$$

ECET 331 - Digital Integrated Circuits

Exclusive OR Gate Electronic Circuit

- Called an **XOR gate**

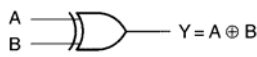

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

ECET 331 - Digital Integrated Circuits



Exclusive NOR Gate

- Two inputs, one output
- Output is HIGH when both inputs are equal – both HIGH or both LOW
- Output is LOW when one, and only one, input is HIGH

ECET 331 - Digital Integrated Circuits

Exclusive NOR Gate Electronic Circuit

- Called an **XNOR gate**

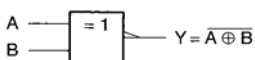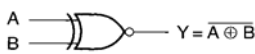

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

ECET 331 - Digital Integrated Circuits


Gate Equivalence - NAND

- A NAND gate can be represented by an AND gate with inverted output
- A NAND gate can be represented by an OR gate with inverted inputs

$$Y = \overline{AB}$$

ECET 331 - Digital Integrated Circuits

Gate Equivalence - NAND

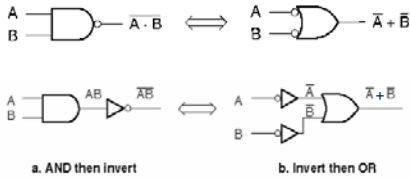

ECET 331 - Digital Integrated Circuits

Gate Equivalence - NOR

- A NOR gate can be represented by an OR gate with inverted output
- A NOR gate can be represented by an AND gate with inverted inputs
- **EXERCISE**

ECET 331 - Digital Integrated Circuits

Gate Equivalence – DeMorgan Forms

- Change an AND function to an OR function and an OR function to an AND function
- Invert the inputs
- Invert the outputs

ECET 331 - Digital Integrated Circuits

DeMorgan's Theorems

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$


ECET 331 - Digital Integrated Circuits

Logic Switches

- Can be used to create logic voltages for circuit inputs
- Provides a logic HIGH or LOW depending on switch position
- Commonly used switches include
 - normally-open pushbutton
 - normally-closed pushbutton
 - single-pole single-throw
 - single-pole double-throw

ECET 331 - Digital Integrated Circuits

Logic Switches

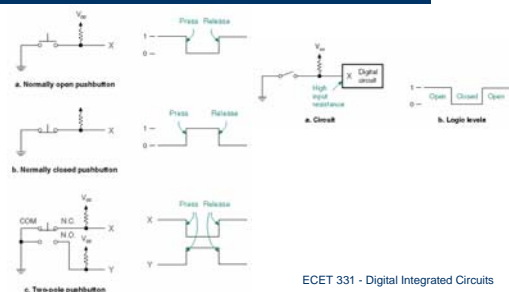

ECET 331 - Digital Integrated Circuits

Light Emitting Diodes (LEDs)

- Conducts current in one direction and only illuminates when it is conducting
- Can be used to monitor outputs of a logic circuit
- Provide a visual indication of a logic state
- Can be wired to display active-HIGH or active-LOW

ECET 331 - Digital Integrated Circuits

LEDs




ECET 331 - Digital Integrated Circuits

LED Operation

- Lights when current flows from anode to cathode
- Use a resistor to avoid burning out the LED with too much current

ECET 331 - Digital Integrated Circuits

LED Circuit

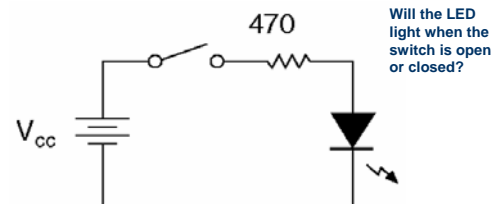

ECET 331 - Digital Integrated Circuits

Logic Gate Enable

- The input to a gate that allows the output to respond to other inputs
- A logic LOW for an OR or NOR gate, a logic HIGH for an AND or NAND gate

ECET 331 - Digital Integrated Circuits


Logic Gate Inhibit

- The input to a gate that forces the output to ignore any other input
- A logic HIGH for an OR or NOR gate, a logic LOW for an AND or NAND gate


ECET 331 - Digital Integrated Circuits

Tristate Buffer

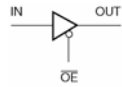- Three output states, HIGH, LOW and high-impedance
- Requires a separate input to control which output state is selected



a. Noninverting

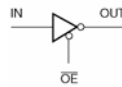


b. Inverting

ECET 331 - Digital Integrated Circuits

Tristate Buffer Applications


- Used to connect multiple outputs together
- Used in controlling the operation of buses

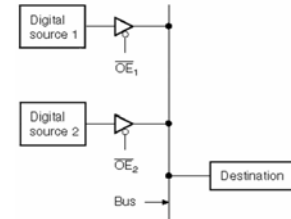

ECET 331 - Digital Integrated Circuits


Integrated Circuit Packages

- Integrated Circuits (ICs) contain many devices in a single package
- Several packaging options are available
- One common package is called dual-in-line package (DIP)

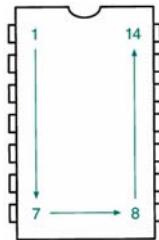

ECET 331 - Digital Integrated Circuits

Other IC Packages

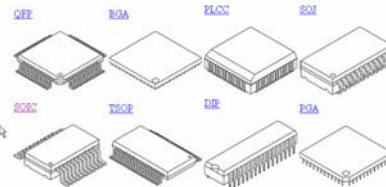

Source: www.adapters.com

ECET 331 - Digital Integrated Circuits

Integrated Circuit Technology

- One common form is transistor-transistor logic, called TTL
- The other common form is Complementary Metal-Oxide Semiconductor, called CMOS

ECET 331 - Digital Integrated Circuits

Integrated Circuit Designation

- Standard form is 74XXNN
 - XX is the logic family designation
 - NN identifies the specific logic function
- See textbook, p. 57

ECET 331 - Digital Integrated Circuits

Terms

- **SSI, MSI, LSI, VLSI**
 - Small, Medium, Large, or Very Large scale Integration depending on the number of gates in an IC package (<12, 12-100, 100-10k, >10k gates)
- **Through-hole**
 - IC packages which are mounted on circuit boards by inserting pins through holes in the board and soldering them in place
- **SMT**
 - Surface Mount Technology – A system of mounting ICs to the surface of a circuit board rather than through-hole

ECET 331 - Digital Integrated Circuits