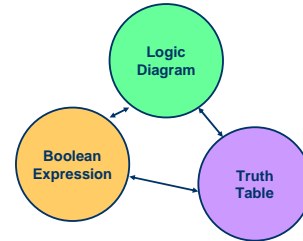


Chapter 3

Boolean Algebra and Combinational Logic

ECET 331 - Digital Integrated Circuits

Objective




ECET 331 - Digital Integrated Circuits

Logic Gate Network

- Two or more logic gates connected together
- Described by truth table, logic diagram or Boolean expression

ECET 331 - Digital Integrated Circuits

Logic Gate Network

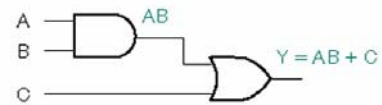

ECET 331 - Digital Integrated Circuits

Boolean Expression from Logic Gate Network

- Similar to finding the expression for a single gate
- Inputs may be compound expressions that represent outputs from previous gates

ECET 331 - Digital Integrated Circuits

Bubble-to-Bubble Convention

- Choose gate symbols so that outputs with bubbles connect to inputs with bubbles
- Results in a cleaner notation and a clearer idea of the circuit function


ECET 331 - Digital Integrated Circuits

Simplification by Double Inversion


- In logic circuits, when two bubbles touch, they cancel out
- In Boolean expressions, bars of the same length cancel

ECET 331 - Digital Integrated Circuits

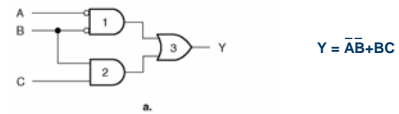Bubble-to-Bubble / Double Inversion (example)



$$Y = \overline{A}B + BC$$

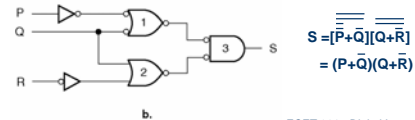

$$S = \overline{\overline{P+Q}}[\overline{Q+R}] \\ = (P+Q)(Q+\overline{R})$$

ECET 331 - Digital Integrated Circuits

Order of Precedence

- Unless otherwise specified, in Boolean expressions AND functions are performed first, followed by ORs

Example: $Y = A \& B + C + D$

- To change the order of precedence, use parentheses

Example: $Y = A \& (B + C + D)$

ECET 331 - Digital Integrated Circuits


Logic Diagrams from Boolean Expressions

- Called *synthesis*
- Use order of precedence
 - A bar over a group of variables is the same as having those variables in parentheses
- Create levels of gating based on orders of precedence

ECET 331 - Digital Integrated Circuits

Logic Diagrams from Boolean Expressions (example)

Synthesize: $Y = (A + B)(C + D)(E + F)$

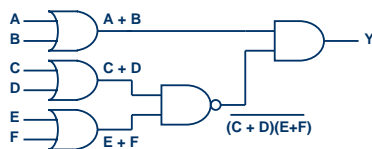

ECET 331 - Digital Integrated Circuits

Truth Tables from Logic Diagrams or Boolean Expressions

- Two methods:
 - 1) Combine individual truth tables from each gate into a final output truth table
 - 2) Develop a Boolean expression and use it to fill in the truth table

Which is more thorough? Which is more efficient?

ECET 331 - Digital Integrated Circuits

Truth Table (Method 1)



A	B	C	$(\bar{A} + \bar{B})$	$(A + C)$	$(\bar{A} + \bar{B})(A + C)$
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	1	0

ECET 331 - Digital Integrated Circuits

Circuit Description Using Boolean Expressions

Definitions:

- A **product term** is a part of a Boolean expression where one or more true or complement variables are **ANDed**
- A **sum term** is a part of a Boolean expression where one or more true or complement variables are **ORed**

ECET 331 - Digital Integrated Circuits

SOP and POS

- A **sum-of-products (SOP)** is a Boolean expression where several product terms are summed (**ORed**) together

Example: $Y = AB + CD + AD$

- A **product-of-sums (POS)** is a Boolean expression where several sum terms are multiplied (**ANDed**) together

Example: $P = (A + B)(C + D)(E + F)$

ECET 331 - Digital Integrated Circuits

Minterms and Maxterms

Minterm

- A product term in a Boolean expression where all possible input variables appear once in true or complemented form

Examples: ABC ; $\bar{A}\bar{B}\bar{C}$

Maxterm

- A sum term in a Boolean expression where all possible variables appear once in true or complemented form

Examples: $(A + B + C)$; $(\bar{A} + \bar{B} + \bar{C})$


ECET 331 - Digital Integrated Circuits

Deriving a SOP Expression from a Truth Table

- Each line of the truth table with a 1 (HIGH) output represents a product term (a minterm) in the truth table's Boolean expression
- Write all input variables for each minterm in true or complement form
 - If an input variable's value is 0, write it in complement form (with a bar over it)
 - If an input variable's value is 1, write it in true form (no bar)
- Combine all minterms as a sum (OR them)

ECET 331 - Digital Integrated Circuits

SOP (example)

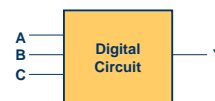

Apply all possible inputs to fill out truth table

Find Minterms:

$\bar{A}\bar{B}\bar{C}$, $\bar{A}BC$, $A\bar{B}\bar{C}$


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

ECET 331 - Digital Integrated Circuits

Bus Form

Bus Form:

A schematic convention in which each variable is available in true or complement form (or *double-rail*) at any point along a conductor

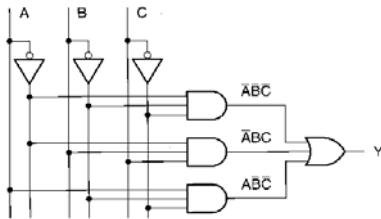


ECET 331 - Digital Integrated Circuits

Deriving a POS Expression from a Truth Table

- 1) Each line of the truth table with a 0 (LOW) output represents a sum term (a maxterm) in the truth table's Boolean expression
- 2) Write all input variables for each maxterm in true or complement form
 - If a variable's value is 1, write it in complement form (with a bar over it)
 - If a variable's value is 0, write it in true form (no bar)
- 3) Combine all maxterms as a product (AND them)

ECET 331 - Digital Integrated Circuits

POS (example)

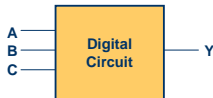

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Apply all possible inputs to fill out the truth table

Find Maxterms:

$(A + B + \bar{C})$, $(A + \bar{B} + C)$, $(\bar{A} + B + \bar{C})$

$(\bar{A} + \bar{B} + C)$, $(\bar{A} + B + \bar{C})$

ECET 331 - Digital Integrated Circuits

Exercise

- Derive the SOP form for an XOR gate

ECET 331 - Digital Integrated Circuits

Theorems of Boolean Algebra

- 24 theorems
- Used to minimize a Boolean expression to reduce the number of logic gates in a network

ECET 331 - Digital Integrated Circuits

Commutative Property

- An operation is commutative if it can be applied to its operands in any order without effecting the result
- AND and OR are commutative
 - Theorem 1: $xy = yx$.
 - Theorem 2: $x + y = y + x$

ECET 331 - Digital Integrated Circuits

Associative Property

- An operation is associative if its operands can be grouped in any order without effecting the result
- AND and OR are associative
 - Theorem 3: $(xy)z = x(yz) = (xz)y$
 - Theorem 4: $(x + y) + z = x + (y + z) = (x + z) + y$

ECET 331 - Digital Integrated Circuits


Distributive Property (of Multiplication over Addition)

- The property allows us to distribute (multiply through) an AND across several OR functions
 - Theorem 5: $x(y + z) = xy + xz$
 - Theorem 6: $(x + y)(w + z) = xw + xz + yw + yz$

ECET 331 - Digital Integrated Circuits

Operations with 1 and 0

- Theorem 7: $x \cdot 0 = 0$
- Theorem 8: $x + 0 = x$
- Theorem 9: $x \oplus 0 = x$
- Theorem 10: $x \cdot 1 = x$
- Theorem 11: $x + 1 = 1$
- Theorem 12: $x \oplus 1 = \bar{x}$

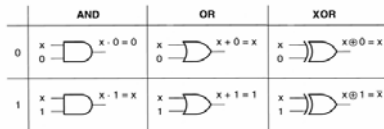

ECET 331 - Digital Integrated Circuits

Operations with One Variable

- The same variable
 - Theorem 13: $x \cdot x = x$
 - Theorem 14: $x + x = x$
 - Theorem 15: $x \oplus x = 0$
- The complement of the variable
 - Theorem 16: $x \cdot \bar{x} = 0$
 - Theorem 17: $x + \bar{x} = 1$
 - Theorem 18: $x \oplus \bar{x} = 1$



ECET 331 - Digital Integrated Circuits

Double Inversion

- Theorem 19: $x = \overline{\overline{x}}$

ECET 331 - Digital Integrated Circuits

DeMorgan's Theorems

- Theorem 20: $\overline{x \cdot y} = \bar{x} + \bar{y}$
- Theorem 21: $\overline{x + y} = \bar{x} \cdot \bar{y}$

ECET 331 - Digital Integrated Circuits

Multivariable Theorems

- Theorem 22: $x + xy = x$
- Theorem 23: $(x + y)(x + z) = x + yz$
- Theorem 24: $x + \overline{xy} = x + y$

ECET 331 - Digital Integrated Circuits

Simplification by Karnaugh Mapping

- A Karnaugh map, called a k-map, is a graphical tool used for simplifying Boolean expressions
- A variation of the Venn diagram

ECET 331 - Digital Integrated Circuits

Construction of a Karnaugh Map

- Square or rectangle divided into cells
- Each cell represents a line in the truth table
- Cell contents are the value of the output variable on that line of the truth table


ECET 331 - Digital Integrated Circuits

K-Map Cell Locations

- Adjacent cells differ by only one variable
- Grouping adjacent cells allows canceling variables in their true and complement forms


ECET 331 - Digital Integrated Circuits

K-Map Forms

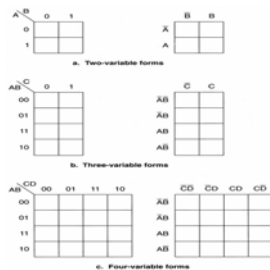

ECET 331 - Digital Integrated Circuits

Other K-Map Forms

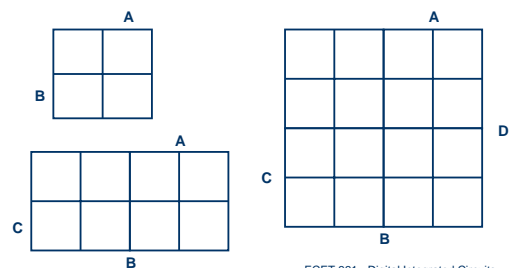

ECET 331 - Digital Integrated Circuits

Loading a K-Map from a Truth Table

- Each line in a truth table has a numerical address according to the binary combination of the inputs
- Each cell in a K-map has a binary address – although not in order due to the need for logical cell adjacency
- Load the cells address of the K-map with the function output for the same line of the truth table

ECET 331 - Digital Integrated Circuits

Loading a K-map from a truth table

A	B	C	#	Y
0	0	0	0	1
0	0	1	1	0
0	1	0	2	0
0	1	1	3	1
1	0	0	4	1
1	0	1	5	0
1	1	0	6	0
1	1	1	7	0

Cell Addresses

		A	
		0	1
C	B	0	1
	0	2	3
1	0	6	7
	1	4	5

Truth Table Outputs

		A	
		1	0
C	B	1	0
	0	0	1
1	0	0	0
	1	0	0

ECET 331 - Digital Integrated Circuits

Grouping Cells

- Cells can be grouped as singles, pairs, quads and octets or hexadectets (i.e. in powers of 2)
- A pair cancels 1 variable
- A quad cancels 2 variables
- An octet cancels 3 variables
- A hexadectet cancels 4 variables

ECET 331 - Digital Integrated Circuits

Grouping Cells (example)

A \ B	0	1
0	1	1
1	0	0

$$Y = \bar{A}$$


ECET 331 - Digital Integrated Circuits

Grouping Cells Along Outside Edges

- The cells along an outside edge are adjacent to cells along the opposite edge
- In a four-variable map, the four corner cells are adjacent

ECET 331 - Digital Integrated Circuits

Grouping Cells Along Outside Edges (example)

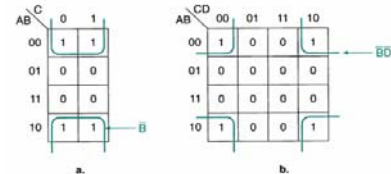

ECET 331 - Digital Integrated Circuits

Multiple Groups

- Each group is a term in the maximum SOP simplified expression
- A cell may be grouped more than once as long as every group has at least one cell that does not belong to any other group


ECET 331 - Digital Integrated Circuits

Don't Care States

- The output state of a circuit for a combination of inputs that will never occur
- We can regard this state as a 1 or 0; whichever will yield maximum simplification
- Shown in a K-map as an "x"

ECET 331 - Digital Integrated Circuits

Don't Care States (example)

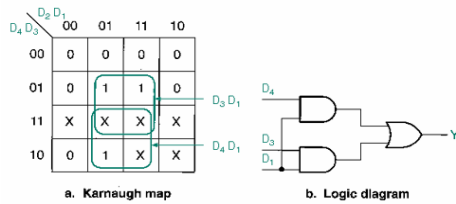

ECET 331 - Digital Integrated Circuits

POS Simplification Using K-maps

- Group those cells with values of 0
- Use the complements of the cell coordinates as the sum term

ECET 331 - Digital Integrated Circuits