

## Chapter 7

### Digital Arithmetic and Arithmetic Circuits

ECET 331 - Digital Integrated Circuits

## Basic Digital Arithmetic

- **Signed binary number**
  - A binary number of fixed length whose sign (+/-) is represented by one bit (usually MSB) and its magnitude by the remaining bits
- **Unsigned binary number**
  - A binary number of fixed length whose sign is not specified by a bit
  - All bits are magnitude and the sign is assumed +

ECET 331 - Digital Integrated Circuits

## Unsigned Binary Arithmetic

- **Sum**
  - Result of an addition operation of two (or more) binary numbers (operands)
    - Augend
    - Addend
- **Carry**
  - A digit (or bit) that is carried over to the next most significant bit during an N-bit addition operation
  - The carry bit is a 1 if the result was too large to be expressed in N bits

ECET 331 - Digital Integrated Circuits

## Basic Rules (Unsigned)

- **One bit unsigned addition**

Cin	A	B	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	1	0	1
1	1	1	1	1

ECET 331 - Digital Integrated Circuits

## Binary Addition (example 1)

$$\begin{array}{r} 1 \\ 10010 \\ + 1010 \\ \hline 11100 \end{array}$$

ECET 331 - Digital Integrated Circuits

## Binary Addition (example 2)

$$\begin{array}{r} 1\ 11111 \\ 10101110 \\ + 10010011 \\ \hline 101000001 \end{array}$$

ECET 331 - Digital Integrated Circuits

## Basic Subtraction

- $X = A - B$ 
  - A = minuend
  - B = subtrahend
  - X = difference or result
  - Requires a borrow bit if  $A < B$
- Other forms of subtraction exist
  - 2's complement addition (used in microprocessors)

ECET 331 - Digital Integrated Circuits

## Basic Subtraction Rules

- One bit unsigned subtraction

Borrow	A	B	Diff
	0	0	= 0
	1	0	= 1
	1	1	= 0
1	0	1	= 1 ( $2_{10} - 1_{10} = 1_{10}$ )

ECET 331 - Digital Integrated Circuits

## Binary Subtraction (example 1)

1110	110(10)	Borrow Stage
<u>- 1001</u>	<u>- 100 1</u>	
?	010 1	
	(14 - 9 = 5)	

ECET 331 - Digital Integrated Circuits

## Binary Subtraction (example 2)

10000	0111(10)	Borrow ripples to LSB
<u>- 101</u>	<u>- 10 1</u>	
?	101 1	
	(16 - 5 = 11)	

ECET 331 - Digital Integrated Circuits

## Signed Binary Numbers

- Sign bit
  - A bit (usually the MSB) that indicates whether a number is positive(=0) or negative (=1)
- Magnitude Bits
  - The bits of a signed binary number that tell how large it is in value

ECET 331 - Digital Integrated Circuits

## Signed Binary Numbers

Note:  
Positive numbers are the same in all three forms

- True Magnitude Form
  - A form of signed binary whose magnitude bits are the TRUE binary form (not complements)
- 1's Complement
  - A form of signed binary in which negative numbers are created by complementing all bits
- 2's Complement
  - A form of signed binary number in which the negative numbers are created by complementing all the bits and adding a 1 (1's Complement + 1)

ECET 331 - Digital Integrated Circuits

## True Magnitude Form

- MSB is the sign bit (Negative: S = 1)
  - Other bits are the magnitude
- 5-bit number examples:

$+25_{10} = 011001$   
 $-25_{10} = 111001$  (Same as +25 with S=1)  
  
 $+12_{10} = 001100$   
 $-12_{10} = 101100$  (Same as +12 with S=1)

ECET 331 - Digital Integrated Circuits

## 1's Complement Form

**1's Complement Form**  
A form of binary number in which negative numbers are generated by complementing all bits of a number including the sign bit

- MSB is the sign bit (Negative: S = 1)
  - Other bits are the magnitude
- 8-bit number examples:

$+57_{10} = 00111001$   
 $-57_{10} = 11000110$  (All bits inverted)  
  
 $+72_{10} = 01001000$   
 $-72_{10} = 10110111$  (All bits inverted)

ECET 331 - Digital Integrated Circuits

## 2's Complement Form

**2's Complement Form**  
A form of binary number in which negative numbers are generated adding 1 to the 1's complement form of the number

- Used in  $\mu P$  arithmetic
- A negative number in 2's complement form can be made positive by 2's complementing it again

$+57 = 00111001$   
 $-57 = 11000110$  (1's comp)  
 $\quad + \quad \underline{\quad 1 \quad}$   
 $\quad 11000111$  (2's comp)  
  
 $+72 = 01001000$   
 $-72 = 10110111$  (1's comp)  
 $\quad + \quad \underline{\quad 1 \quad}$   
 $\quad 10110110$  (2's comp)

ECET 331 - Digital Integrated Circuits

## Signed Binary Addition

- Done in the same way as unsigned addition except...
  - Both operands must have the same number of magnitude bits
  - Both operands must have a sign bit
- Positive: Sign = 0

$+30: \quad 00011110$   
 $+75: \quad + \underline{01001011}$   
 $+105: \quad 01101001$

ECET 331 - Digital Integrated Circuits

## Signed Binary Subtraction

- Using complement notation, we can add a negative number rather than subtracting a positive number
  - Same circuitry for both operations
  - This does not work for true magnitude numbers

ECET 331 - Digital Integrated Circuits

## 1's Complement Subtraction

- Add the 1's complement and then add any carry

$+80_{10} = 01010000$   
 $+65_{10} = 01000001$   
 $-65_{10} = 10111110$  (1's comp)  
  
 $80 \quad 01010000$   
 $-65 \quad + \underline{10111110}$   
 $\quad 1 \quad 00001110$   
 $\quad + \quad \underline{\quad 1 \quad}$  (End around carry)  
 $+15 \quad 00001111$

ECET 331 - Digital Integrated Circuits

## 2's Complement Subtraction

- Add the 2's complement to the minuend

$$\begin{array}{r}
 +80_{10} = 01010000 \\
 +65_{10} = 01000001 \\
 -65_{10} = 10111110 \text{ (1's complement)} \\
 + \quad \quad \quad 1 \\
 \hline
 -65_{10} = 10111111 \text{ (2's complement)}
 \end{array}$$

- If a carry results, discard it

$$\begin{array}{r}
 80 \quad 01010000 \\
 -65 \quad + 10111111 \\
 +15 \quad 1\ 00001111 \text{ (Discard the carry)}
 \end{array}$$

ECET 331 - Digital Integrated Circuits

## Negative Sum or Difference

- If True Magnitude Form is used for subtraction, results will be incorrect
- If the results from a 1's complement or 2's complement is negative (S=1), the magnitude is found by taking the complement of the result

ECET 331 - Digital Integrated Circuits

## Negative Sum or Difference

$$\begin{array}{r}
 +65: \quad 0100\ 0001 \\
 -80: \quad + 1011\ 0000 \text{ (2's C.)} \\
 \quad \quad 1111\ 0001 \text{ (Negative sum)} \\
 \quad \quad 0000\ 1110 \text{ (Invert)} \\
 \quad \quad + \quad \quad 1 \text{ (Add 1)} \\
 \quad \quad 0000\ 1111 \text{ (Final Answer: 15, negative)}
 \end{array}$$

ECET 331 - Digital Integrated Circuits

## Range of Signed Numbers

- Range of positive numbers is 0 to  $2^N - 1$  for an N-bit magnitude
- Range of negative numbers is -1 to  $-2^N$  for an N-bit magnitude
- Example: 8-bit range (i.e. 7-bit magnitude)  
( $-2^7 < x < 2^7 - 1$ ) or ( $-128 < x < 127$ )

ECET 331 - Digital Integrated Circuits

## Exercise

- Write  $-16_{10}$  as an 8-bit 2's complement number

$$\begin{array}{r}
 +16 = 00010000 \\
 -16 = 11101111 \text{ (1's C.)} \\
 + \quad \quad \quad 1 \text{ (Add 1)} \\
 \hline
 11110000 \text{ (2's C.)}
 \end{array}$$

ECET 331 - Digital Integrated Circuits

## Sign Bit Overflow

- Overflow
  - A erroneous carry into the sign bit of a signed binary number that results from a sum or difference that is larger than can be represented by the magnitude bits
- Results in a false positive or a false negative number

ECET 331 - Digital Integrated Circuits

## False Negative Overflow

- 8-bit addition

- Two positive numbers added with a result greater than +127 for 8-bit numbers causes an overflow

```
+75: 01001011
+96: + 01000001
-----
10101011 (negative - False)
```

ECET 331 - Digital Integrated Circuits

## False Positive Overflow

- Addition of two 8-bit negative numbers

- Two positive numbers added with a result greater than +127 for 8-bit numbers causes an overflow

```
-80: 10110000 (2's C.)
-65: + 10111111 (2's C.)
-----
01101111 (positive - False)
```

A sum of 2 positive numbers is always positive. A sum of 2 negative numbers is always negative. Any 2's complement arithmetic which contradicts this has produced an overflow in the sign bit.

ECET 331 - Digital Integrated Circuits

## Hexadecimal Addition

- Similar to decimal addition with additional digits A – F

F + 1 = 10  
F + F = 1E  
F + F + 1 = 1F

- Easier than working with large binary numbers

ECET 331 - Digital Integrated Circuits

## BCD Codes

- Binary Coded Decimal
  - A code used to represent each decimal digit of a number by a 4-bit binary value
  - Valid Digits for 0-9 are (0000 to 1001) the binary codes 1010 to 1111 are invalid
  - Called an 8421 Code due to the decimal weight of each bit position

ECET 331 - Digital Integrated Circuits

## BCD (examples)

$4987_{10} = 0100\ 1001\ 1000\ 0111$  (BCD)

$84_{10} = 1000\ 0100$  (BCD)

Each digit is a 4 Bit Binary group

ECET 331 - Digital Integrated Circuits

## Gray Code

- A binary code that progresses such that only one bit changes between two successive codes

Decimal	True Binary	Gray Code
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

- Generated as
  - $g_3 = b_3$
  - $g_2 = b_3 \text{ xor } b_2$
  - $g_1 = b_2 \text{ xor } b_1$
  - $g_0 = b_1 \text{ xor } b_0$

- Very useful in hardware design

ECET 331 - Digital Integrated Circuits

## ASCII Code

- American Standard Code for Information Interchange
- A seven bit alphanumeric code used to represent text letters, numerals, punctuation, and special controls
- An expanded 8 bit form is often used also
  - Allows for some graphical characters

ECET 331 - Digital Integrated Circuits

## Binary Adders

- Half Adder(HA): A circuit that will add two bits and produce a sum and carry result
- Full Adder(FA): A circuit that will add a carry bit from another HA or FA (previous stage) and two operand bits to produce a sum and carry result

ECET 331 - Digital Integrated Circuits

## Basic HA Addition

- One bit addition rules
  - Three possible combinations

$0 + 0 = 00$   
 $0 + 1 = 01$   
 $1 + 1 = 10$

ECET 331 - Digital Integrated Circuits

## HA Circuit


- Basic Equations  
(S = Sum, C = Carry)

- $S = A \text{ xor } B$
- $C = A \text{ and } B$

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


ECET 331 - Digital Integrated Circuits

## HA Circuit and Symbol

 

ECET 331 - Digital Integrated Circuits

## Full Adder

 

ECET 331 - Digital Integrated Circuits

## Full Adder

- Adds a  $C_{in}$  to the HA

- Basic Equations:


$$C_{out} = (A \text{ xor } B)C_{in} + AB$$

$$S = (A \text{ xor } B) \text{ xor } C_{in}$$

A	B	$C_{in}$	$C_{out}$	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


ECET 331 - Digital Integrated Circuits

## FA Circuit

 


ECET 331 - Digital Integrated Circuits

## FA Circuit (Using HAs)

 

ECET 331 - Digital Integrated Circuits

## Parallel (N-bit) Binary Adder

 


ECET 331 - Digital Integrated Circuits

## Ripple Carry

- In the N-Bit Parallel Adder (FA Stages) the  $C_{OUT}$  is generated by the last stage ( $FA_N$ )
- This is called a Ripple Carry Adder because the final  $C_{OUT}$  (Last Stage) is based on a ripple through each stage by  $C_{IN}$  at the LSB Stage

ECET 331 - Digital Integrated Circuits

## Ripple Carry

 

Text: figure 7.11

ECET 331 - Digital Integrated Circuits

## Ripple Carry

- Each Stage will have a propagation delay on the  $C_{IN}$  to  $C_{OUT}$  of one AND gate and one OR gate
- A 4-Bit ripple carry adder will then have a propagation delay on the final  $C_{OUT}$  of  $4 \times 2 = 8$  gates
- A 32 Bit adder such as in a  $\mu P$  in a PC could have a delay of 64 Gates

ECET 331 - Digital Integrated Circuits

## Fast Carry (or Look-Ahead Carry)

- A combinational network that generates the final  $C_{OUT}$  directly from the operand bits ( $A_1$  to  $A_N$ ,  $B_1$  to  $B_N$ )
- It is independent of the operations of each FA Stage (unlike the ripple carry)

ECET 331 - Digital Integrated Circuits

## Fast (Look-Ahead) Carry

- Has a small propagation delay compared to the ripple carry
- Delay is 3 gates for a 4-bit adder compared to 8 for the ripple carry

ECET 331 - Digital Integrated Circuits

## Subtractor (2's Complement)

- Subtraction using 2's complement addition allows use of parallel FAs
- The subtract operation involves adding the inverse of the subtrahend to the minuend and then add a 1


ECET 331 - Digital Integrated Circuits

## Subtraction (2's Complement)

- Difference =  $A - B = A + !B + 1$
- This operation can be done in a parallel N-Bit FA by Inverting  $B_1$  through  $B_N$  and connecting  $C_{IN}$  at the LSB Stage to +5V (adding 1)
- The circuit can be modified to allow either the ADD or SUBTRACT operation to be performed

ECET 331 - Digital Integrated Circuits

## XOR as Programmable Inverter

 

XOR as a Programmable Inverter – (See Text pp.381-382)

ECET 331 - Digital Integrated Circuits



## Adder / Subtractor

- See Dueck for Figure 7.15


ECET 331 - Digital Integrated Circuits

## BCD Adder (1)

- A parallel adder whose output sum is in groups of 4 bits each representing a BCD (8421) digit
- Basic design is a 4-bit binary parallel adder to generate a 4-bit sum of  $A + B$
- Sum is input to the four bit input of a  $B_{IN}$  to BCD code converter

ECET 331 - Digital Integrated Circuits

## BCD Adder (2)

 

- Standard binary adder with a code converter
- If the sum is greater than 9, add 6 to convert to BCD
- Greater than 9 if  $\Sigma 1$  and  $\Sigma 3$  or  $\Sigma 2$

ECET 331 - Digital Integrated Circuits

## BCD Code Converter

- Code converter design is based on the 4-bit adder used with [Table 7.11 in the text](#)
- The complete design is shown in Fig. 7.26
- The  $A_i$  inputs of the code converter adder are fixed to be either a 0000 ( $C=0$ ) or 0110 ( $C=1$ ). The 0110 corrects binary overflow to BCD

ECET 331 - Digital Integrated Circuits

## Entity Example

### 2-to-4 decoder

```
ENTITY decodel IS
    PORT(D1,D0 : IN BIT;
          Y0,Y1,Y2,Y3 : OUT BIT);
END decodel;
```

ECET 331 - Digital Integrated Circuits

## Architecture Example

```
ARCHITECTURE behavioral OF decodel IS
BEGIN
    Y0 <= (not D1) and (not D0);
    Y1 <= (not D1) and (D0);
    Y2 <= (D1) and (not D0);
    Y3 <= (D1) and (D0);
END decoder;
```

ECET 331 - Digital Integrated Circuits

## Another Entity Format

```
ENTITY decode1 IS
  PORT(D : IN  STD_LOGIC_VECTOR(1 downto 0);
        Y : OUT STD_LOGIC_VECTOR(3 downto 0));
END decode1;
```

ECET 331 - Digital Integrated Circuits

## Another Entity Format

- This format groups signals of similar purpose
- into a **bus** (or **vector**)
- Instead of D1, D0 we use D(1 downto 0)
- Instead of Y3, Y2, Y1, Y0, we use Y(3 downto 0)

ECET 331 - Digital Integrated Circuits

## Selected Signal Assignments

- Uses a VHDL construct called WITH SELECT
- Basic Format  
WITH (my\_vector) SELECT
- The selected signal state is used to determine the output changes

ECET 331 - Digital Integrated Circuits

## Architecture Using Selected Signal Assignment

```
ARCHITECTURE behavioral OF decode1 IS
  BEGIN
    WITH (D) SELECT
      Y <= "0001" WHEN "00",
           "0010" WHEN "01",
           "0100" WHEN "10",
           "1000" WHEN "11",
           "0000" WHEN OTHERS;
  END decoder;
```

ECET 331 - Digital Integrated Circuits

## Seven Segment Decoder Entity

```
ENTITY bcd_7seg IS
  PORT( d3, d2, d1, d0 : IN  BIT;
        a,b,c,d,e,f,g : OUT BIT);
END bcd_7seg;
-- Defines binary inputs d0 to d3
-- Defines 7 outputs a to g
```

ECET 331 - Digital Integrated Circuits

## Seven Segment Decoder (CA) Architecture

```
ARCHITECTURE seven_segment OF bcd_7seg IS
  SIGNAL input : BIT_VECTOR(3 downto 0);
  SIGNAL output : BIT_VECTOR(6 downto 0);
  BEGIN
    input <= D3 & D2 & D1 & D0
    -- Uses two intermediate signals called
    -- input and output (internal no pins)
    -- Creates an array by using the concatenate
    -- operator (&) In this case input(3) <= D3,
    -- input(2) <= D2 etc.
```

ECET 331 - Digital Integrated Circuits

## SS (CA) Architecture Internal States

```
WITH input SELECT
  output <= "0000001" WHEN "0000",
  output <= "1001111" WHEN "0001",
  output <= "0010010" WHEN "0010",
  output <= "0000110" WHEN "0011",
  output <= "1001100" WHEN "0100",
  output <= "0100100" WHEN "0101",
  ...
  output <= "1111111" WHEN OTHERS;
```

ECET 331 - Digital Integrated Circuits

## SS Architecture Outputs

```
a <= output(6);
b <= output(5);
c <= output(4);
d <= output(3);
e <= output(2);
f <= output(1);
g <= output(0);
END seven_segment;
```

Intermediate signal  
output(6 downto 0) is  
mapped to ports a - g

ECET 331 - Digital Integrated Circuits

## VHDL Sequential Process

- A **process** is a VHDL construct which encloses statements which are to be evaluated sequentially
- A process is executed when a signal in a **sensitivity list** changes

```
PROCESS(Sensitivity List)
BEGIN
  Sequential Statements;
END PROCESS;
```

ECET 331 - Digital Integrated Circuits

## Ripple Blanking Process (3)

- Process steps are evaluated in order:
  - First IF-THEN statements
  - Then CASE statements
  - and so on until END PROCESS;

ECET 331 - Digital Integrated Circuits

## IF-THEN-ELSE

- IF-THEN-ELSE statements are used for conditional testing on certain inputs or signals
- Used extensively in HDLs and sequential logic
- Implies priority

ECET 331 - Digital Integrated Circuits

## Priority Encoder Architecture

```
ARCHITECTURE prioenc OF enc3to8 IS
BEGIN
  Q(2) <= D(7) OR D(6) OR D(5) OR D(4);
  Q(1) <= D(7) OR D(6) OR ((not D(5)) and
    (not D(4)) and D(3))
    OR ((not D(5)) and (not D(4)) and D(2));
  Q(0) <= -- In a similar fashion
END prioenc;
```

ECET 331 - Digital Integrated Circuits

## Another Encoder Form

- WHEN-ELSE is similar to IF-THEN-ELSE

```
BEGIN
  Q <= 7 WHEN D(7) = '1' ELSE
    6 WHEN D(6) = '1' ELSE
    5 WHEN D(5) = '1' ELSE
    4 WHEN D(4) = '1' ELSE
    3 WHEN D(3) = '1' ELSE
    2 WHEN D(2) = '1' ELSE
    |
    |
    0;
```

ECET 331 - Digital Integrated Circuits

## 4-to-1 Mux Architecture

```
ARCHITECTURE mux4tol OF mux4 IS
BEGIN
  PROCESS(S) -- Process is sensitive to S (S1,S0) Selects
  BEGIN
    CASE S IS
      WHEN "00" => Y <= D(0);
      WHEN "01" => Y <= D(1);
      WHEN "10" => Y <= D(2);
      WHEN "11" => Y <= D(3);
      WHEN OTHERS => Y <= '0';
    END CASE;
  END PROCESS;
END mux4tol;
```

ECET 331 - Digital Integrated Circuits

## 4-Bit Magnitude Comparator Architecture

```
ARCHITECTURE behavioral OF mag4 IS
  SIGNAL compare : STD_LOGIC_VECTOR(2 downto 0);
BEGIN
  PROCESS (ai,bi) -- Sensitive to Ai and Bi Integer Arrays
  BEGIN
    IF ai < bi THEN compare <= "110";
    ELSIF ai = bi THEN compare <= "101";
    ELSIF ai > bi THEN compare <= "011";
    ELSE compare <= "111";
    END IF;

    agtb <= compare(2);
    aeqb <= compare(1);
    altb <= compare(0);
  END PROCESS;
END mag4;
```

ECET 331 - Digital Integrated Circuits

## Parity Generator (6-Bit) Architecture

```
ARCHITECTURE behavioral OF pargen IS
BEGIN
  parity <= A0 XOR A1 XOR A2 XOR A3 XOR A4 XOR A5;
END behavioral;
```

ECET 331 - Digital Integrated Circuits

## Structured VHDL (Terms)

- Hierarchy
  - A group of design entities associated in a series of levels (the hierarchy) in which complete designs form portions or subsections of the upper design
- Component
  - A complete VHDL Design Entity that can be used as part of a higher level file in a hierarchical design

ECET 331 - Digital Integrated Circuits

## Structured VHDL (Terms)

- Port
  - An input or output of a VHDL design entity or component
- Component Declaration
  - A statement that defines the IO port names of a component in a VHDL design entity
- Instantiate
  - To use an instance of a component


ECET 331 - Digital Integrated Circuits

## Structured VHDL (Terms)

- Component Instantiation
  - A statement that maps the port names of a VHDL component to port names, internal signals, or variables of a higher level VHDL design entity
  - Also called a PORT MAP

ECET 331 - Digital Integrated Circuits

## Structured VHDL (example)

 

ECET 331 - Digital Integrated Circuits

## Full Adder VHDL Entity

```
ENTITY full_add IS
  PORT( a, b, cin :IN BIT;
        cout, sum :OUT BIT);
END full_add;
```

ECET 331 - Digital Integrated Circuits

## Full Adder VHDL Architecture

```
ARCHITECTURE adder OF full_add IS
  BEGIN
    cout <= ((a XOR b) AND cin) OR (a AND b);
    sum <= (a XOR b) XOR cin;
  END adder;
```

ECET 331 - Digital Integrated Circuits

## 4-Bit Parallel Adder Entity

```
ENTITY add4par IS
  PORT( c0 :IN BIT;
        a, b :IN BIT_VECTOR(4 downto 1);
        c4 :OUT BIT;
        sum :OUT BIT_VECTOR(4 downto 1));
END add4par;
```

ECET 331 - Digital Integrated Circuits

## 4-Bit Parallel Adder Component

```
COMPONENT full_add -- Previous FA Design Entity
  PORT( a, b, cin :IN BIT;
        cout, sum :OUT BIT);
END COMPONENT

SIGNAL c :BIT_VECTOR(3 downto 1)
-- Internal signal used for intermediate carries
```

ECET 331 - Digital Integrated Circuits

## 4-Bit Parallel Adder

- This design uses the 1-bit FA as a Component to create the 4-bit parallel adder
- The basic adder component is mapped four times uses a component instantiation such as adder1, adder2, etc.
- The connections are set as a PORT MAP for each instance of the component

ECET 331 - Digital Integrated Circuits

## 4-Bit Adder Structured Architecture

```
BEGIN
adder1: full_add -- This defines the first component
  PORT MAP(a => A(1), b=> B(1), cin => C(0),
    cout => C(1), sum=> SUM(1));
adder2: full_add -- This defines the second component
  PORT MAP(a => A(2), b=> B(2), cin => C(1),
    cout => C(2), sum=> SUM(2));
adder3: full_add -- This defines the third component
  PORT MAP(a => A(3), b=> B(3), cin => C(2),
    cout => C(3), sum=> SUM(3));
adder4: full_add -- This defines the fourth component
  PORT MAP(a => A(4), b=> B(4), cin => C(3),
    cout => C4, sum=> SUM(4));
END adder;
```

ECET 331 - Digital Integrated Circuits

## Other Structures

- The preceding example mapped directly to 4 FA components
- Another approach would be to use a VHDL repetitive loop construct called a GENERATE statement
- This is similar to a FOR loop with an index variable
- Both types are still ripple-carry adders

ECET 331 - Digital Integrated Circuits

## 4-Bit Adder Architecture with GENERATE Statement

```
ARCHITECTURE adder of add4gen IS
  COMPONENT full_add
    PORT ( a, b, cin : IN BIT;
      cout, sum : OUT BIT );
  SIGNAL c : BIT_VECTOR (4 downto 0);
BEGIN
  C(0) <= C0;
  FOR i IN 1 to 4 GENERATE
    adders: full_add PORT MAP( a(i), b(i), C(i-1), C(i), sum(i) );
  END GENERATE;
END adder;
```

ECET 331 - Digital Integrated Circuits