

AC Analysis of a Common-Emitter Amplifier

The Common-Emitter Amplifier is used to achieve high voltage gain and employs a bi-junction transistor (BJT). A diagram of the common-emitter amplifier is shown in figure 1.

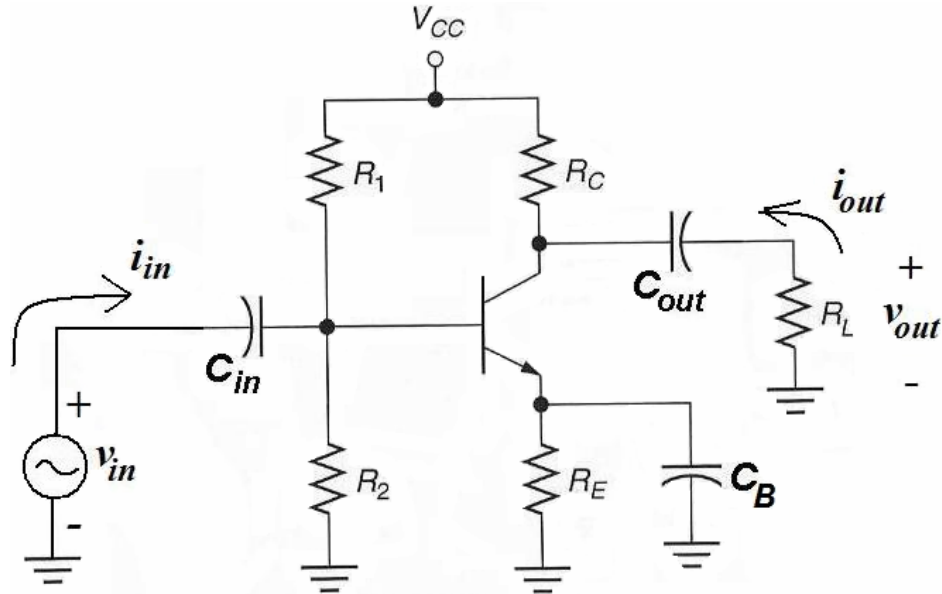


Figure 1. Common emitter (CE) amplifier circuit

Parameter definitions:

R_1, R_2 = Voltage Divider Resistors

R_C = Collector Resistor

R_E = Emitter Resistor

I_B = DC Base Current

I_C = DC Collector Current

I_E = DC Emitter Current

V_B = DC Base Voltage

V_C = DC Collector Voltage

V_E = DC Emitter Voltage

V_{BE} = DC Base-Emitter Voltage

V_{CC} = DC Supply Voltage

$$h_{FE} = \text{DC Current Gain} = \frac{I_C}{I_B}$$

v_{in} = AC input voltage

i_{in} = AC input current

v_{out} = AC output voltage

i_{out} = AC output current

The AC analysis of the common emitter amplifier involves replacing the transistor with its AC equivalent circuit, shown in figure 2.

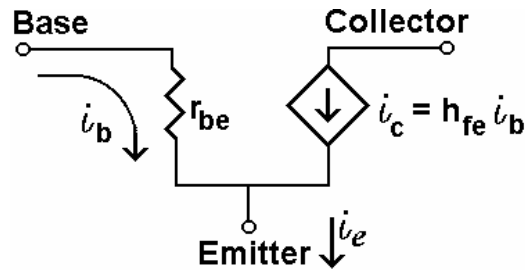


Figure 2. AC equivalent circuit of a bi-junction transistor

The parameters of this equivalent circuit are:

i_b = AC base current

i_c = AC collector current h_{fe} = AC Current Gain = $\frac{i_c}{i_b}$

i_e = AC emitter current r_{be} = Internal AC resistance of the base-emitter junction

The value of the AC current gain (h_{fe}) is typically fairly close to the DC current gain (h_{FE}). The AC resistance of the base-emitter junction (r_{be}) is calculated from:

$$r_{be} = \frac{0.025}{I_E} \quad \text{where } I_E = \text{DC Emitter Current}$$

Since this is a superposition problem, we short out the DC power supply VCC in Figure 1, and connect the AC equivalent circuit in Figure 2. We also short out all capacitors, because they will be selected to assure AC shorts over the frequency range of the input voltage, v_{in} . The result is the AC equivalent circuit of the entire amplifier shown in figure 3.

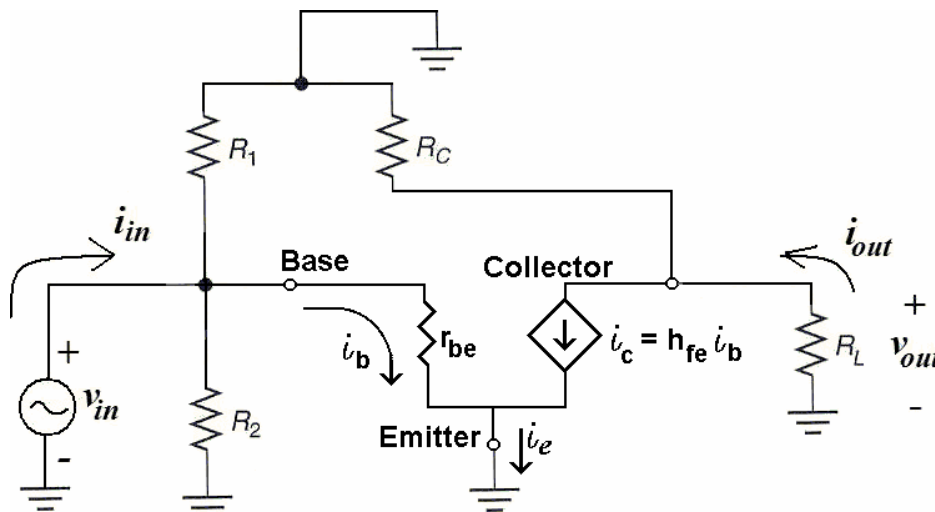


Figure 3. AC equivalent circuit of the common emitter (CE) amplifier

The circuit in Figure 3 can be simplified to that shown in figure 4.

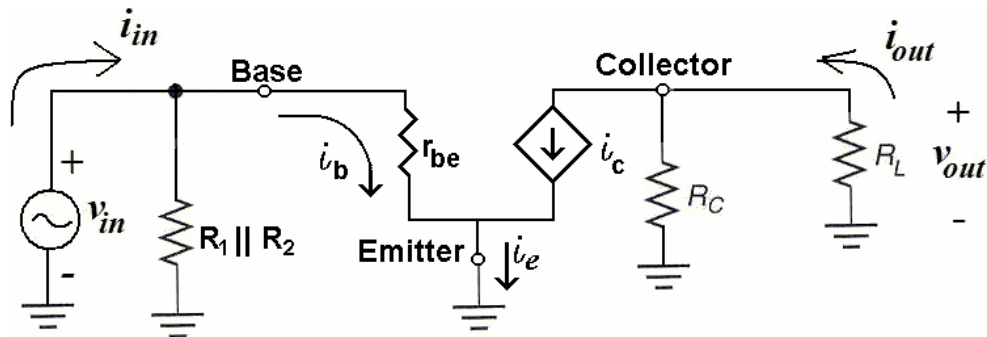


Figure 4. AC equivalent circuit of the common emitter (CE) amplifier

DC Analysis.

Given the amplifier parameters:

V_{BE} = DC Base-Emitter Voltage

V_{CC} = DC Supply Voltage

h_{FE} = DC Current Gain

h_{fe} = AC Current Gain

R_1 = First Voltage Divider Resistor

R_2 = Second Voltage Divider Resistor

R_C = Collector Resistor

I_E = DC Emitter Current

Compute the voltage gain $A_v = \frac{v_{out}}{v_{in}}$

The AC resistance of the base-emitter junction (r_{be}) is calculated from:

$$r_{be} = (h_{fe} + 1) \left(\frac{0.025}{I_E} \right) \quad (1)$$

By Ohm's law, the AC base current is $i_b = \frac{v_{in}}{r_{be}}$ (2)

The AC collector current is $i_c = h_{fe} i_b$ (3)

The AC collector current is pulled through the parallel combination of R_C and R_L . So by Ohm's Law, the output voltage is:

$$v_{out} = i_c (R_C \parallel R_L) \quad (4)$$

Example 1. Given the amplifier parameters:

$$V_{BE} = 0.7 \text{ V}$$

$$V_{CC} = 12 \text{ V}$$

$$v_{in} = 10 \text{ mV rms}$$

$$H_{FE} = H_{fe} = 100$$

$$R_1 = 10000$$

$$R_2 = 5000$$

$$R_C = 2000$$

$$R_E = 1000$$

$$R_L = 5000$$

Compute the voltage gain $A_v = \frac{v_{out}}{v_{in}}$

Solution:

From Example 1 in the DC analysis handout, we computed the DC emitter current to be:

$$I_E = 3.195 \text{ mA} \quad (\text{P1.1})$$

The AC resistance of the base-emitter junction (r_{be}) is calculated from:

$$r_{be} = (h_{fe} + 1) \left(\frac{0.025}{I_E} \right) = (100 + 1) \left(\frac{0.025}{0.0003195} \right) = (101)(7.825 \Omega) = 790.3 \Omega$$

By Ohm's law, the AC base current is $i_b = \frac{v_{in}}{r_{be}} = \frac{0.01}{790.3} = 0.00001265 = 12.65 \mu\text{A rms}$

The AC collector current is

$$i_c = h_{fe} i_b = (100)(12.65 \times 10^{-6}) = 1265 \times 10^{-6} = 1.265 \times 10^{-3} = 1.265 \text{ mA rms}$$

The AC output voltage is:

$$\begin{aligned} v_{out} &= i_c (R_C \parallel R_L) = (1.265 \text{ mA rms})(2000 \parallel 5000) \\ &= (1.265 \text{ mA rms}) \left(\frac{(2000)(5000)}{2000 + 5000} \Omega \right) \\ &= (1.265 \text{ mA rms}) \left(\frac{10000000}{7000} \Omega \right) \\ &= (1.265 \text{ mA rms})(1429 \Omega) \\ &= (1808 \text{ mV rms}) = 1.808 \text{ V rms} \end{aligned}$$

The voltage gain is $A_v = \frac{v_{out}}{v_{in}} = \frac{1808 \text{ mV rms}}{10 \text{ mV rms}} = 181$