

## DC Analysis of a Common-Emitter Amplifier

The Common-Emitter Amplifier is used to achieve high voltage gain and employs a bi-junction transistor (BJT). A diagram of the common-emitter amplifier is shown in figure 1.

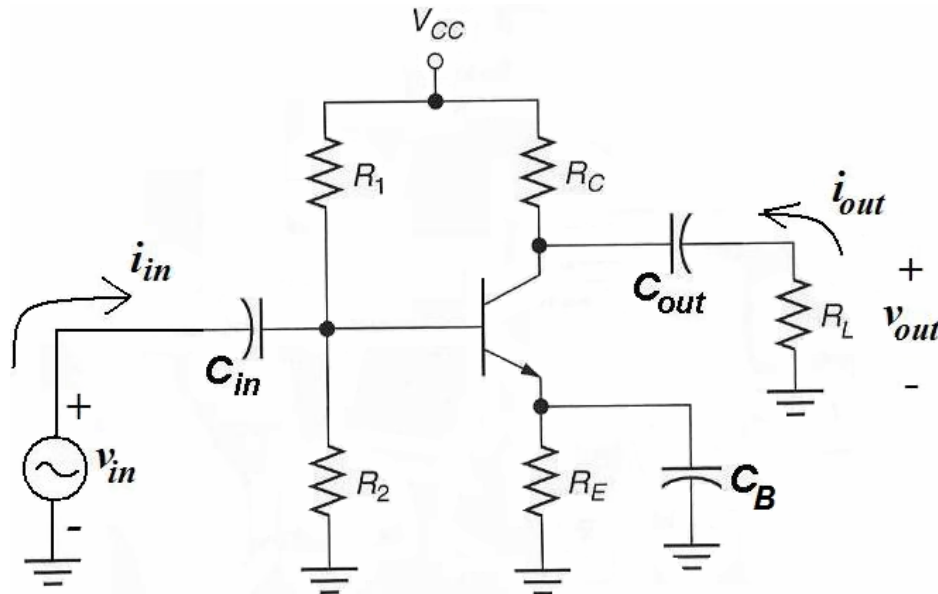


Figure 1. Common emitter (CE) amplifier circuit

The AC voltage  $v_{in}$  is provided by an audio source such as a microphone or an MP3 player.

The resistance  $R_L$  is the load resistance of the next amplifier stage, or could be the resistance of an audio speaker.

One purpose of  $C_{in}$  is to prevent DC current from flowing from  $V_{cc}$  to  $v_{in}$ , and thus preventing damage to the audio source. Another purpose of  $C_{in}$  is to provide an AC short between  $v_{in}$  and the base of the transistor, allowing AC current  $i_{in}$  to freely flow through the capacitor.

The purpose of  $C_{out}$  is to prevent DC current from flowing from  $V_{cc}$  to  $v_{out}$ . This will prevent damage to the audio speaker or it will prevent DC loading effects on the next amplifier stage. Another purpose of  $C_{out}$  is to provide an AC short between the collector of the transistor and the load resistance, allowing AC current  $i_{out}$  to freely flow through the capacitor.

### **DC Analysis.**

For DC analysis, we can remove all capacitors, since there is no DC current through them. The DC equivalent circuit is shown in Figure 2.

Parameter definitions:

$I_B$  = DC Base Current

$I_C$  = DC Collector Current

$I_E$  = DC Emitter Current

$V_B$  = DC Base Voltage

$V_C$  = DC Collector Voltage

$V_E$  = DC Emitter Voltage

$V_{BE}$  = DC Base-Emitter Voltage

$V_{CC}$  = DC Supply Voltage

$h_{FE}$  = DC Current Gain =  $\frac{I_C}{I_B}$

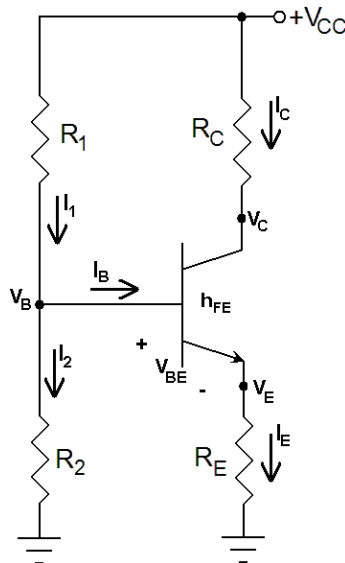


Figure 2. DC equivalent circuit of a common emitter amplifier

About transistor amplifiers When a transistor is operating as an amplifier, the DC current gain ( $h_{FE}$ ) is a given constant value. The typical values for  $h_{FE}$  range from 75 to 200, depending on the type of BJT. For the 2N3904, which is a very commonly used BJT  $h_{FE}$  is typically about 150. Another characteristic of a correctly operation transistor amplifier is that the base-emitter voltage ( $V_{BE}$ ) is about 0.7 volts.

The resistors  $R_1$  and  $R_2$  form a voltage divider to provide a stable base voltage. One can test to see if the voltage divider is working correctly by removing the transistor and measuring the base voltage. A stable circuit is achieved if the base voltage is about the same whether or not the transistor is in the circuit.

DC analysis:

Given the amplifier parameters:

$V_{BE}$  = DC Base-Emitter Voltage  
 $V_{CC}$  = DC Supply Voltage  
 $h_{FE}$  = DC Current Gain  
 $R_1$  = First Voltage Divider Resistor  
 $R_2$  = Second Voltage Divider Resistor  
 $R_C$  = Collector Resistor  
 $R_E$  = Emitter Resistor

Compute the electrical quantities

$I_B$  = DC Base Current  
 $I_C$  = DC Collector Current  
 $I_E$  = DC Emitter Current  
 $V_B$  = DC Base Voltage  
 $V_C$  = DC Collector Voltage  
 $V_E$  = DC Emitter Voltage

By Ohm's law, the emitter voltage is  $V_E = I_E R_E$  (1)

By KVL, the base voltage is  $V_B = V_{BE} + V_E$  (2)

Substituting (2) into (1) gives us  $V_B = V_{BE} + I_E R_E$  (3)

Let's assume the transistor is operating correctly with a base-emitter voltage ( $V_{BE}$ ) is about 0.7 volts. Therefore, the base voltage is:

$$V_B = 0.7 + I_E R_E \quad (4)$$

The transistor currents obey KCL:

$$I_E = I_B + I_C \quad (5)$$

Substituting  $I_C = h_{FE} I_B$  into (5) gives us

$$\begin{aligned} I_E &= I_B + h_{FE} I_B \\ &= I_B (h_{FE} + 1) \end{aligned} \quad (6)$$

Substituting (6) into (4) yields

$$\begin{aligned} V_B &= 0.7 + V_E \\ &= 0.7 + I_B (h_{FE} + 1) R_E \end{aligned} \quad (7)$$

Ohm's law for the base voltage through resistor  $R_2$  is:

$$V_B = I_2 R_2 \quad (8)$$

Equating (7) with (8) yields

$$I_2 R_2 = 0.7 + I_B (h_{FE} + 1) R_E \quad (9)$$

By KCL, the base current can be expressed as:

$$I_B = I_1 - I_2 \quad (10)$$

Substituting (10) into (9), yields

$$I_2 R_2 = 0.7 + (I_1 - I_2)(h_{FE} + 1) R_E \quad (11)$$

We can arrange (11) into the form,  $aI_1 + bI_2 = c$ , as follows:

$$\begin{aligned} I_2 R_2 &= 0.7 + (I_1 - I_2)(h_{FE} + 1) R_E \\ &= 0.7 + (I_1)(h_{FE} + 1) R_E - (I_2)(h_{FE} + 1) R_E \end{aligned} \quad (12)$$

Group current terms of the left side to obtain

$$-I_1(h_{FE} + 1) R_E + I_2 R_2 + I_2(h_{FE} + 1) R_E = 0.7 \quad (13)$$

Simplify left side to obtain

$$-I_1(h_{FE} + 1) R_E + I_2(R_2 + (h_{FE} + 1) R_E) = 0.7 \quad (14)$$

KVL from  $V_{CC}$  through  $R_1$  and  $R_2$  yields

$$I_1 R_1 + I_2 R_2 = V_{CC} \quad (15)$$

Equations (14) and (15) form a system of two equations and two unknowns ( $I_1$  and  $I_2$ ). These can be formed into a matrix equation:

$$\begin{bmatrix} -(h_{FE} + 1) R_E & R_2 + (h_{FE} + 1) R_E \\ R_1 & R_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.7 \\ V_{CC} \end{bmatrix} \quad (16)$$

The matrix equation can be solved by inverting the resistance matrix:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -(h_{FE} + 1) R_E & R_2 + (h_{FE} + 1) R_E \\ R_1 & R_2 \end{bmatrix}^{-1} \begin{bmatrix} 0.7 \\ V_{CC} \end{bmatrix}$$

A 2x2 matrix

$$A = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

has an inverse of

$$A^{-1} = \frac{1}{ad - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

**Example 1.** Given the amplifier parameters:

$$V_{BE} = 0.7 \text{ V}$$

$$V_{CC} = 12 \text{ V}$$

$$h_{FE} = 100$$

$$R_1 = 5000$$

$$R_2 = 10000$$

$$R_C = 2000$$

$$R_E = 1000$$

Compute the electrical quantities

$I_B$  = DC Base Current

$I_C$  = DC Collector Current

$I_E$  = DC Emitter Current

$V_B$  = DC Base Voltage

$V_C$  = DC Collector Voltage

$V_E$  = DC Emitter Voltage

$V_{\text{Divider}}$  = DC Voltage at the base of the voltage divider if the transistor is removed.

Solution:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -(h_{FE} + 1)R_E & R_2 + (h_{FE} + 1)R_E \\ R_1 & R_2 \end{bmatrix}^{-1} \begin{bmatrix} 0.7 \\ V_{CC} \end{bmatrix}$$

Substitute given parameters:

$$\begin{aligned} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} &= \begin{bmatrix} -(100 + 1)1000 & 5000 + (100 + 1)1000 \\ 10000 & 5000 \end{bmatrix}^{-1} \begin{bmatrix} 0.7 \\ 12 \end{bmatrix} \\ &= \begin{bmatrix} -(101)1000 & 5000 + (101)1000 \\ 10000 & 5000 \end{bmatrix}^{-1} \begin{bmatrix} 0.7 \\ 12 \end{bmatrix} \\ &= \begin{bmatrix} -101000 & 106000 \\ 10000 & 5000 \end{bmatrix}^{-1} \begin{bmatrix} 0.7 \\ 12 \end{bmatrix} \end{aligned} \quad (\text{P1.1})$$

The 2x2 resistor matrix

$$R = \begin{bmatrix} a & b \\ c & d \end{bmatrix} = \begin{bmatrix} -101000 & 106000 \\ 10000 & 5000 \end{bmatrix}$$

has an inverse of

$$\begin{aligned} R^{-1} &= \frac{1}{ad - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix} \\ &= \frac{1}{(-101000)(5000) - (106000)(10000)} \begin{bmatrix} 5000 & -106000 \\ -10000 & -101000 \end{bmatrix} \\ &= \frac{1}{(-505000000) - (1060000000)} \begin{bmatrix} 5000 & -106000 \\ -10000 & -101000 \end{bmatrix} \\ &= \frac{1}{-1.565e9} \begin{bmatrix} 5000 & -106000 \\ -10000 & -101000 \end{bmatrix} \end{aligned} \quad (\text{P1.2})$$

Substituting (P1.2) into (P1.1) yields

$$\begin{aligned}
 \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} &= \begin{bmatrix} -101000 & 106000 \\ 10000 & 5000 \end{bmatrix}^{-1} \begin{bmatrix} 0.7 \\ 12 \end{bmatrix} \\
 &= \frac{1}{-1.565e9} \begin{bmatrix} 5000 & -106000 \\ -10000 & -101000 \end{bmatrix} \begin{bmatrix} 0.7 \\ 12 \end{bmatrix} \\
 &= \frac{1}{-1.565e9} \begin{bmatrix} (5000)(0.7) + (-106000)(12) \\ (-10000)(0.7) + (-101000)(12) \end{bmatrix} \\
 &= \frac{1}{-1.565e9} \begin{bmatrix} (3500) + (-1272000) \\ (-7000) + (-1212000) \end{bmatrix} \\
 &= \frac{1}{-1.565e9} \begin{bmatrix} -1268500 \\ -1219000 \end{bmatrix} \\
 &= \begin{bmatrix} -1268500 / -1.565e9 \\ -1219000 / -1.565e9 \end{bmatrix} = \begin{bmatrix} 810.543 \\ 778.914 \end{bmatrix} \times 10^{-6}
 \end{aligned}$$

Therefore, we have the voltage divider currents  $I_1 = 810.543 \mu\text{A}$  and  $I_2 = 778.914 \mu\text{A}$ .

The base current is computed from (10):

$$I_B = I_1 - I_2 = 810.543 - 778.914 = 31.629 \mu\text{A}$$

The collector current is computed from the base current:

$$\begin{aligned}
 I_C &= h_{FE} I_B = (100)(31.629 \mu\text{A}) \\
 &= (3162.9 \mu\text{A}) = 3.163 \text{mA}
 \end{aligned}$$

The emitter current is computed from KCL (5):

$$I_E = I_B + I_C = 31.629 \mu\text{A} + 3162.9 \mu\text{A} = 3195 \mu\text{A} = 3.195 \text{mA}$$

The emitter voltage is computed from Ohms's Law (1):

$$V_E = I_E R_E = (3.195 \text{mA})(1000 \Omega) = 3195 \text{mV} = 3.195 \text{V}$$

The base voltage is computed from KVL (2):

$$V_B = V_{BE} + V_E = 0.7 + 3.195 = 3.895 \text{V}$$

The collector voltage is computed from KVL:

$$\begin{aligned}
 V_C &= V_{CC} - I_C R_C = 12 \text{V} - (3.163 \text{mA})(2000 \Omega) \\
 &= 12 \text{V} - 6326 \text{mV} = 12 \text{V} - 6.326 \text{V} = 5.674 \text{V}
 \end{aligned}$$

If one removes the transistor, the voltage at the base of the voltage divider is

$$V_{\text{Divider}} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{5000}{10000 + 5000} \right) (12V)$$

$$= \left( \frac{5000}{15000} \right) (12V) = \left( \frac{1}{3} \right) (12V) = 4V$$

This is a good result, because it compares favorably with the transistor base voltage of 3.895 volts. This shows that the transistor amplifier will be stable.

The MATLAB program shown in figure 4 implements the Matrix equation (16) and some other equations above to compute all the transistor currents and voltages, given the circuit parameters of a common-emitter amplifier. A sample execution is shown in figure 3. Notice that the results given in figure 3 match the solution provided above for Example 1.

```

***** Common Emitter Amplifier *****
Given Parameters
*****
Resistor R1          = 10000 ohms
Resistor R2          = 5000 ohms
Collector Resistor   = 2000 ohms
Emitter Resistor     = 1000 ohms
*****

***** DC Analysis *****
Base Voltage          = 3.89 volts
Unloaded Base Voltage = 4.00 volts
Collector Voltage     = 5.67 volts
Emitter Voltage       = 3.19 volts
Base Current          = 31.63 uA
Collector Current     = 3.16 mA
Emitter Current       = 3.19 mA
*****

```

Figure 3. Sample MATLAB program execution

```

% Common Emitter Amplifier with voltage divider bias
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
%           Input parameters
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
Re = 1000; % emitter resistance in ohms
R1 = 10000; % voltage divider resistance R1 in ohms
R2 = 5000; % voltage divider resistance R2 in ohms
hFE = 100; % DC current gain
Rc = 2000; % collector resistance in ohms
Vcc = 12; % DC power supply voltage in volts

fprintf('***** Common Emitter Amplifier *****\n');
fprintf('           Given Parameters           \n');
fprintf('           *****\n');
fprintf(' Resistor R1           = %d ohms\n', R1);
fprintf(' Resistor R2           = %d ohms\n', R2);
fprintf(' Collector Resistor    = %d ohms\n', Rc);
fprintf(' Emitter Resistor      = %d ohms\n', Re);
fprintf('*****\n');

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
%           DC Analysis
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

% set up matrix equation
R = [-(hFE+1)*Re      R2+(hFE+1)*Re;
     R1              R2];
V = [0.7
     Vcc];

% Solve matrix equation
I = inv(R)*V ;
I1 = I(1); % current in resistor R1
I2 = I(2); % current in resistor R2

% Compute transistor currents and voltages
Ib = I1 - I2; % base current
Ic = b*Ib; % collector current
Ie = Ib+Ic; % emitter current
Ve = Ie*Re; % emitter voltage
Vb = Ve+0.7; % base voltage
Vc = Vcc - Ic*Rc; % collector voltage
VbUnloaded = Vcc*R2/(R1+R2); % base voltage with BJT removed

% results
fprintf('\n***** DC Analysis Results *****\n');
fprintf(' Base Voltage           = %.2f volts\n', Vb);
fprintf(' Unloaded Base Voltage  = %.2f volts\n', VbUnloaded);
fprintf(' Collector Voltage      = %.2f volts\n', Vc);
fprintf(' Emitter Voltage        = %.2f volts\n', Ve);
fprintf(' Base Current           = %.2f uA\n', Ib*1e6);
fprintf(' Collector Current      = %.2f mA\n', Ic*1000);
fprintf(' Emitter Current        = %.2f mA\n', Ie*1000);
fprintf('*****\n');

```

Figure 4. MATLAB program for the DC analysis of a common emitter amplifier