

## Homework 8

- 1) There is no energy stored in the  $15\mu F$  and  $5\mu F$  capacitors at the time the switch is closed in the circuit of Fig.1.  
 Find (a) the initial value  $v(0)$ , (b) the final value  $v(\infty)$ , (c) the time constant  $\tau$ , and (d) the expressions  $v(t)$  and  $i(t)$  for  $t \geq 0$ .

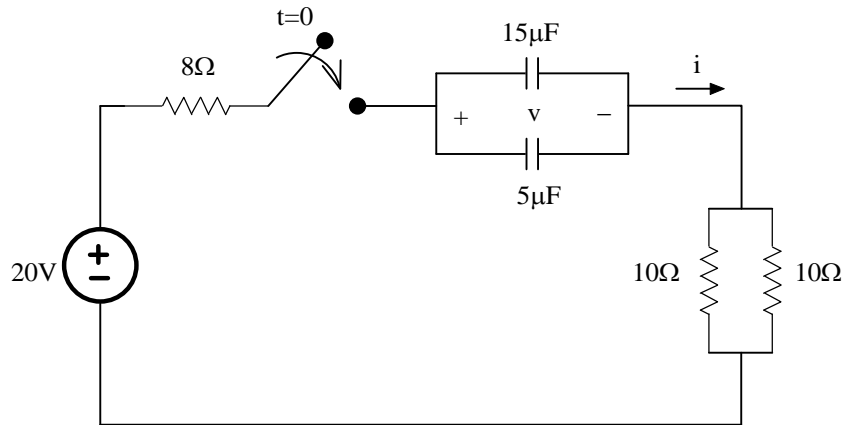


Fig.1.

- 2) In the circuit of Fig.2, the voltage and current expressions are

$$v(t) = 40e^{-\alpha t} \quad (\text{V}), \quad \text{for } t \geq 0^+$$

$$i(t) = 4e^{-\alpha t} \quad (\text{A}), \quad \text{for } t \geq 0$$

where  $\alpha = 5$  (1/sec).

Find (a) the resistance  $R$ , (b) the time constant  $\tau$ , (c) the inductance  $L$ , (d) the initial energy stored in the inductor.

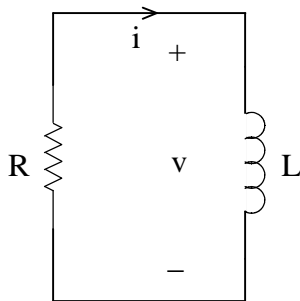


Fig.2.

- 3) The switch in the circuit of Fig.3 has been closed for a long time before opening at  $t = 0$ . Find (a) the initial voltage across the capacitor  $v(0)$ , (b) the time constant  $\tau$ , (c) the voltage  $v(t)$  for  $t \geq 0$ , (d) the initial energy stored in the capacitor.

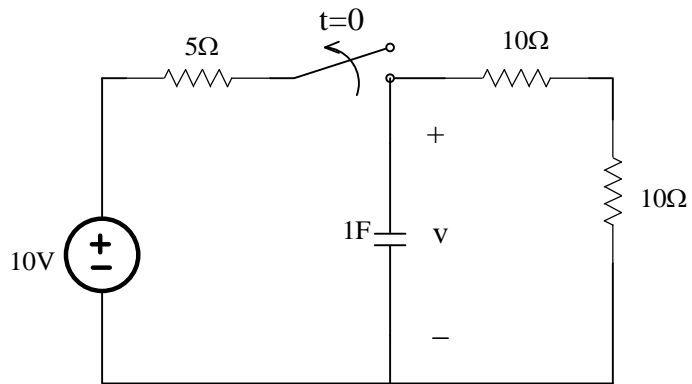


Fig.3.