

EE202 Homework 3

- (1) A load consisting of a $1350\ \Omega$ resistor in parallel with a $405\ \text{mH}$ inductor is connected across the terminals of a voltage source $v = 90\cos(2500t)$ (V). Find
- (a) the peak value of the instantaneous power delivered by the source.
 - (b) the average power delivered to the load.
 - (c) the reactive power delivered to the load.
 - (d) the power factor of the load.
 - (e) the reactive factor of the load.

- (2) Find the average power, the reactive power, and the apparent power absorbed by the load in the circuit shown below if $i = 30\cos(100t)$ (mA).

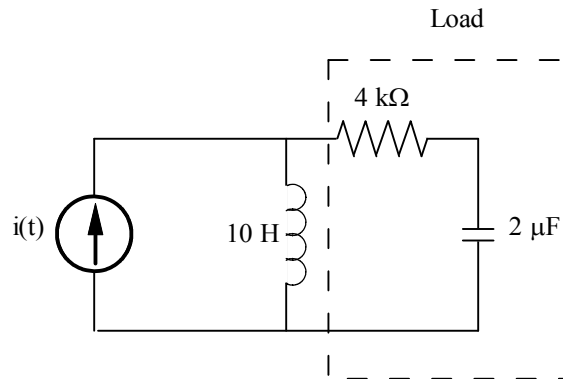


Fig.2