

EE202 Homework 8

- (1) Use the Fourier transform to find  $v_0(t)$  and  $i_0(t)$  in the circuit in Fig. 1 if  $v_g = 15 \operatorname{sgn}(t)$  (V).

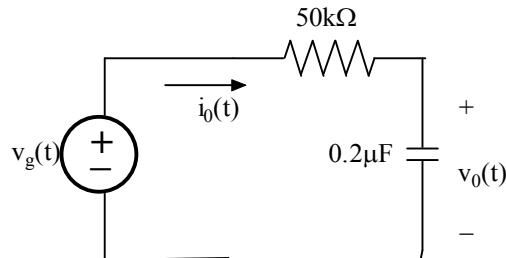


Fig. 1.

- (2) Use the Fourier transform to find  $v_0(t)$  and  $i_0(t)$  in the circuit in Fig. 2 if  $i_g = 2 \operatorname{sgn}(t)$  (A).

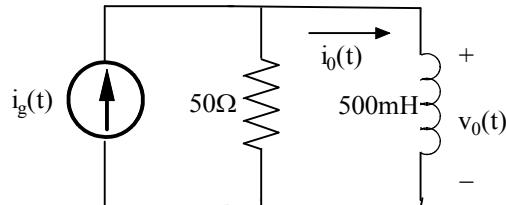


Fig. 2.

- (3) Find the impedance  $Z_{in}$  in Fig. 3 if  $Z_L = 100 + j200 \Omega$ .

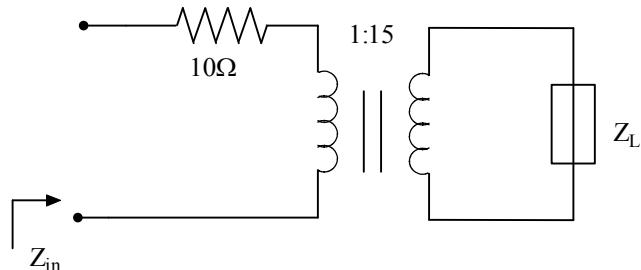


Fig. 3.