

EE202 Homework 10

- (1) For the balanced Y-Y system shown in Fig.1, the line has an impedance of  $10-j5 \text{ } (\Omega)$ , the load impedance is  $90+j5 \text{ } (\Omega)$ . Suppose that the phase sequence is positive, and  $V_{an} = 110\sqrt{2}\angle 0^\circ \text{ (v)}$ . Determine the line voltages  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$ , the phase current  $I_{AN}$  and the phase voltage  $V_{AN}$ .

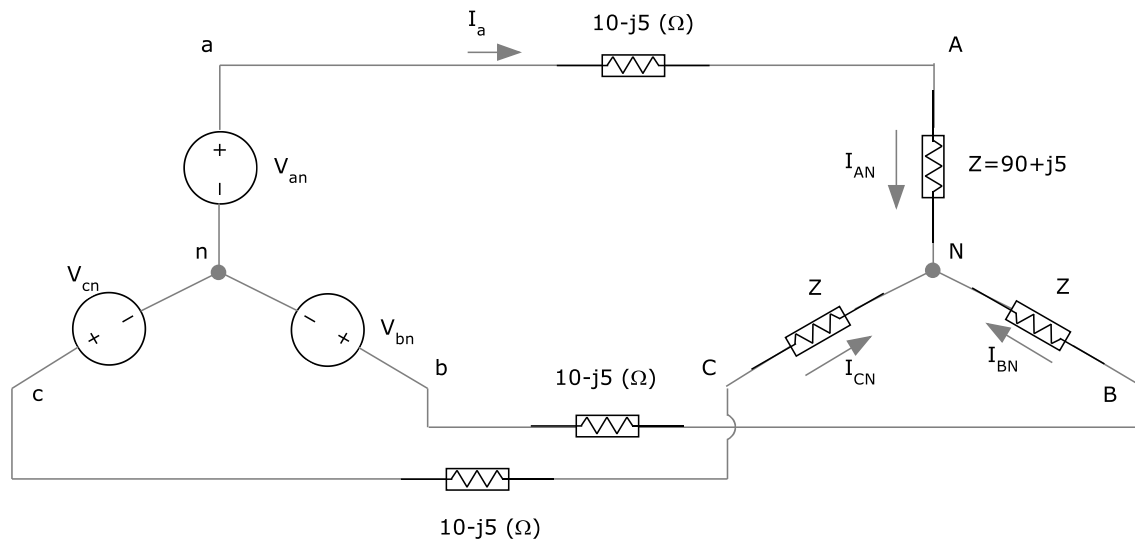


Fig. 1

- (2) For the balanced Y- $\Delta$  system shown in Fig.2, the load impedance is  $Z = 10+j10 \text{ } (\Omega)$ . Suppose that the phase sequence is positive, and  $V_{an} = 110\sqrt{2}\angle 0^\circ \text{ (v)}$ . Determine the phase currents  $I_{AB}$ ,  $I_{CA}$  and the line current  $I_a$ .

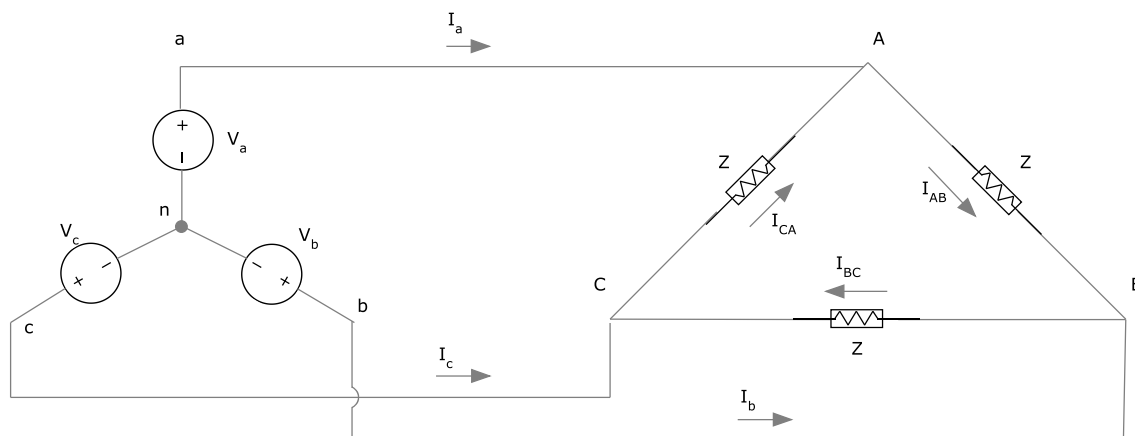


Fig. 2