

Practice Problem-A Answer Key

1 (a): $I = -0.0976$ (A), (b): $I = -0.188$ (A), (c): $I = -0.927$ (A), (d): $I = 1.143$ (A)

2 (a): $V = 11.7$ (V), (b): $V = 8.89$ (V), (c): $V = 0.587$ (V)

3 $R_x = 600$ (Ω)

4 $I = 0.35$ (A)

5 $I = 0.2$ (A)